

March 18



**Induction and
Inductance
Chapter 31**

Review - Self Inductance

- > Self-induced emf, \mathcal{E}_L appears in any coil in which the current is changing

$$\mathcal{E}_L = -L \frac{di}{dt}$$

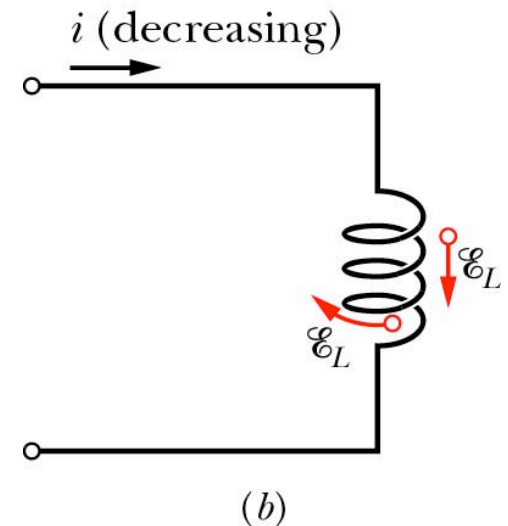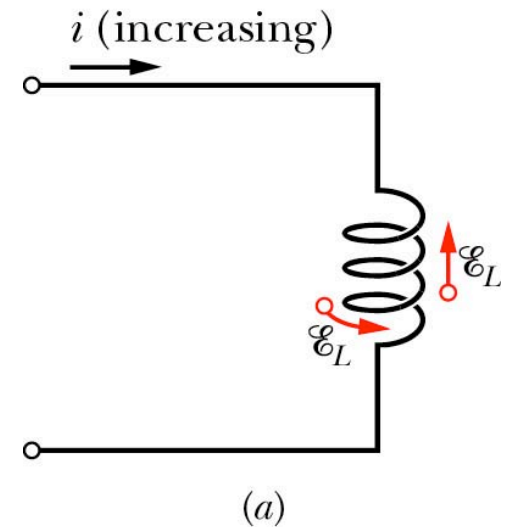- > Direction of \mathcal{E}_L follows Lenz's law and opposes the change in current




Review - Mutual Inductance

- > What is induced emf in coil 1 from a changing current in coil 2?

$$\mathcal{E}_1 = -M \frac{di_2}{dt}$$

where
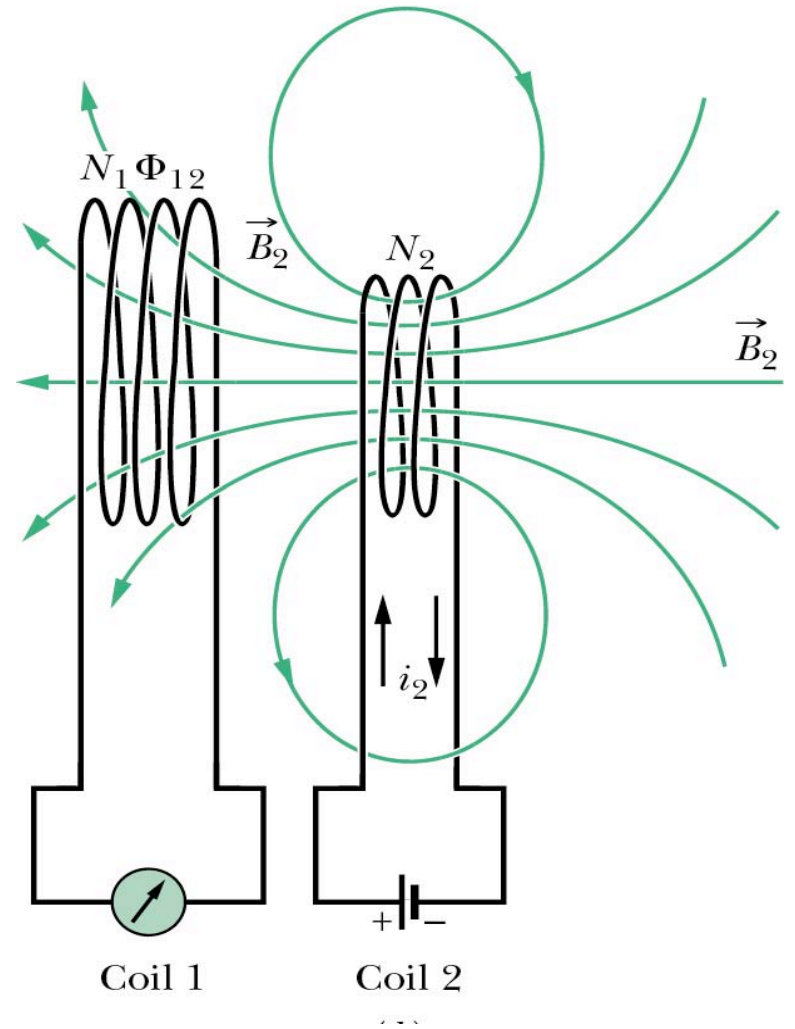
$$M = \frac{N_1 \Phi_{12}}{i_2} = \frac{N_2 \Phi_{21}}{i_1}$$



Review: RC circuit

> **RC circuit** is a resistor and capacitor in series


- Charging up a capacitor (switch at a)
- Kirchhoff rule for loop:

$$\frac{dq}{dt}R + \frac{q}{C} - \mathcal{E} = 0$$

(=differential equation)

- Solution

$$q = C\mathcal{E}(1 - e^{-t/\tau_c})$$

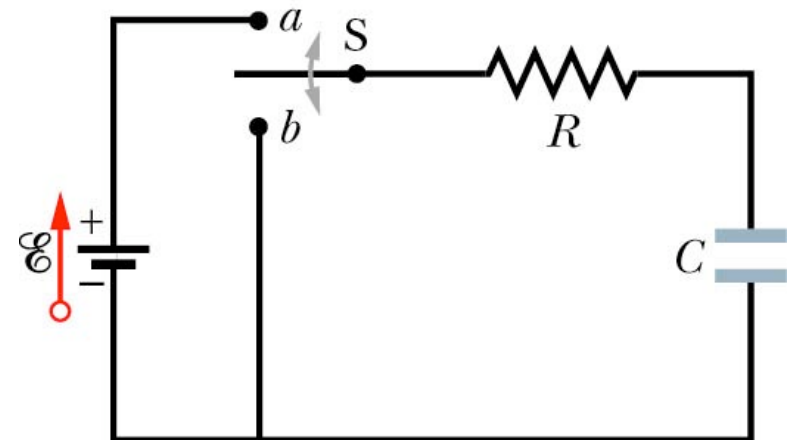

- Discharging capacitor (switch at b)

$$q = q_0 e^{-t/\tau_c}$$


Inductance

- > **RL circuit** is a resistor and inductor in series
- > Close switch to point **a**
 - o **Initially** i is increasing through inductor so \mathcal{E}_L opposes rise and i through R will be


$$i < \mathcal{E} / R$$

- o **Long time later**, i is constant so $\mathcal{E}_L = 0$ and i in circuit is

$$i = \mathcal{E} / R$$


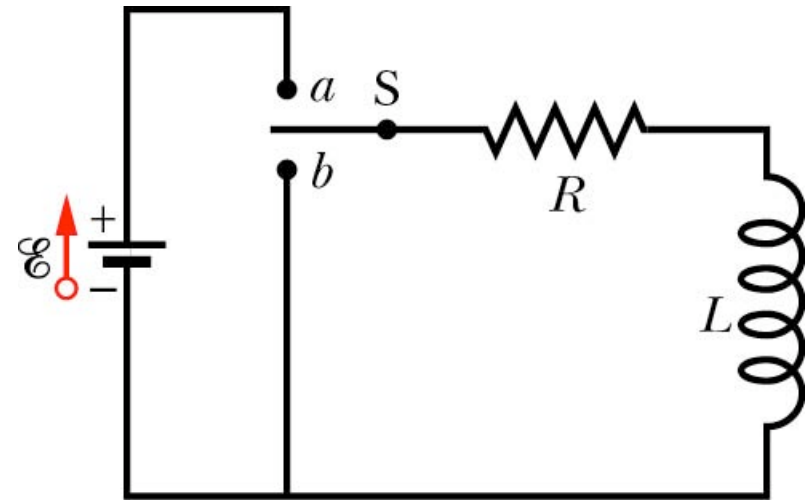


$$\mathcal{E}_L = -L \frac{di}{dt}$$

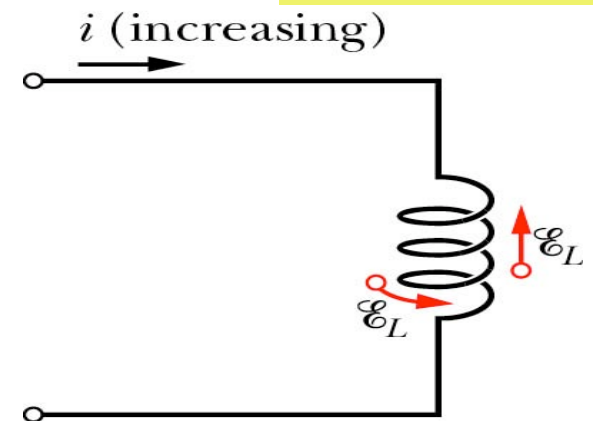

RL Circuit - Differential Equation

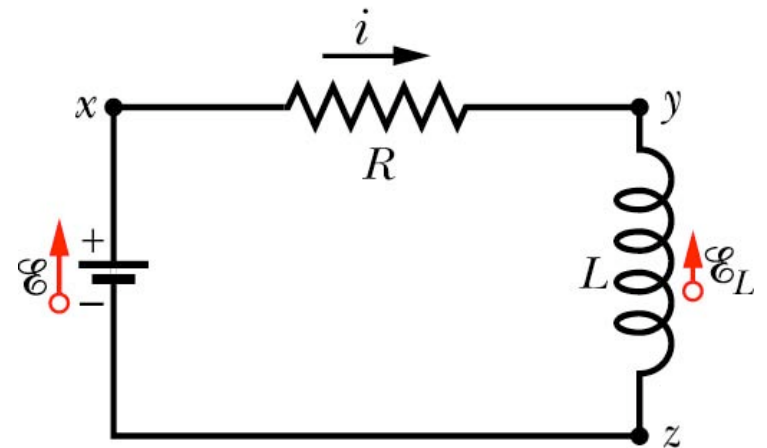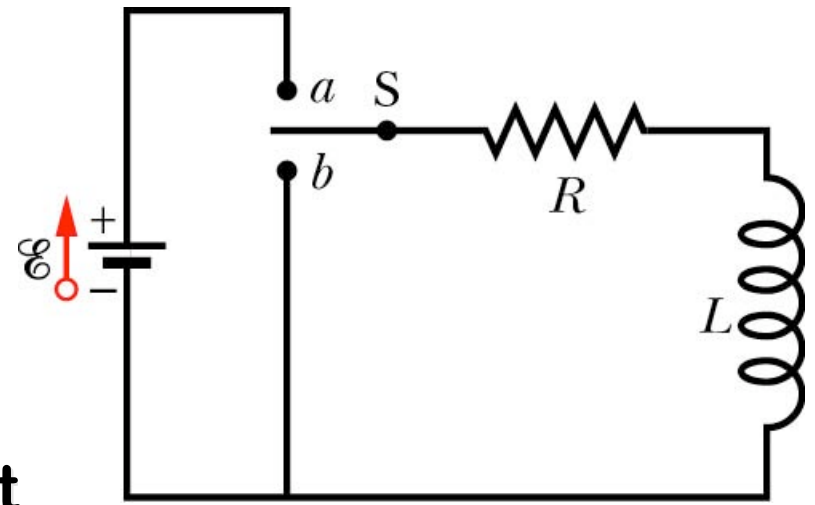- > Initially an inductor acts to oppose changes in current through it
- > Long time later inductor acts like ordinary conducting wire
- > Apply Kirchhoff loop rule right after switch has been closed at *a*



$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

RL Circuit Solution

- > Differential equation similar to RC circuit:

$$L \frac{di}{dt} + iR - \mathcal{E} = 0$$


$$\frac{dq}{dt} R + \frac{q}{C} - \mathcal{E} = 0$$

- > Solution is

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L} \right)$$

- > Inductive time constant is

$$\tau_L = \frac{L}{R}$$

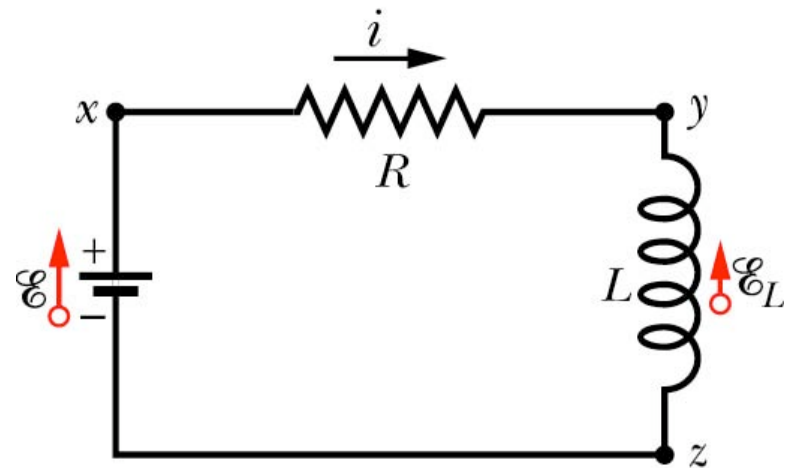

- > Satisfies conditions:

- o At $t=0$, $i = 0$
- o At $t=\infty$, $i = \mathcal{E}/R$


“Discharging”=Stop Current

- > Now move switch to position b so battery is out of system
- > Current will decrease with time and loop rule gives

$$iR + L \frac{di}{dt} = 0$$

- > Solution is
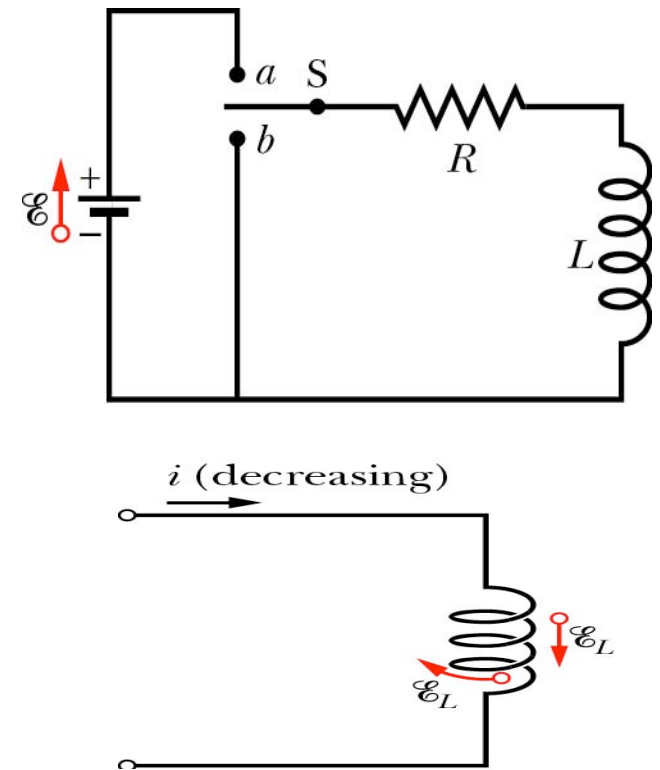
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



- > Satisfies conditions

- o At $t=0$, $i = i_0 = \mathcal{E}/R$
- o At $t=\infty$, $i = 0$

RL circuits Summary


- Circuit is closed (switch to “a”)

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau_L} \right)$$

- Circuit is opened (switch to “b”)

$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$

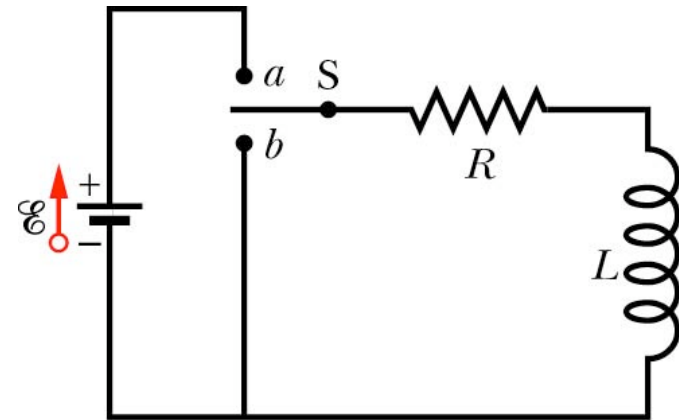- Time constant is $\tau_L = \frac{L}{R}$





Switch at **a**, current through inductor is:

- > Initially $i = 0$ (acts like **broken wire**)
- > Long time later $i = \mathcal{E}/R$ (acts like **simple wire**)

Problem 31-5

- > Have a circuit with resistors and inductors
- > What is the current through the battery **just after** closing the switch?
- > Inductor oppose change in current through it
- > Right after switch is closed, current through inductor is 0
- > **Inductor acts like broken wire**

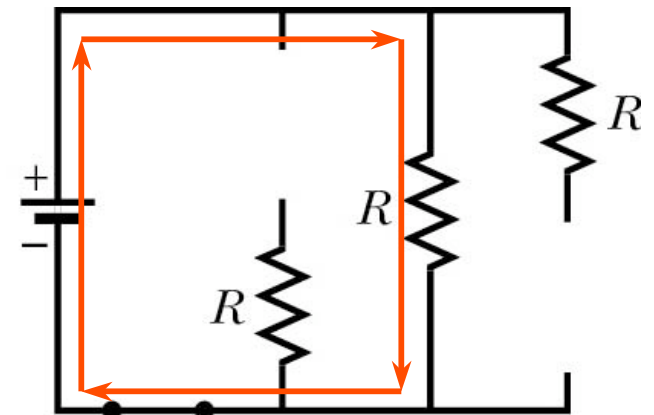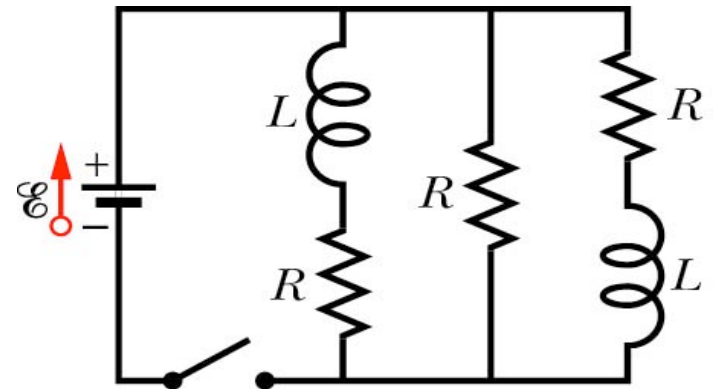



Problem 31-5, continued

- > Apply loop rule

$$\mathcal{E} - iR = 0$$


- > Immediately after switch closed, current through the battery is

$$i = \frac{\mathcal{E}}{R}$$

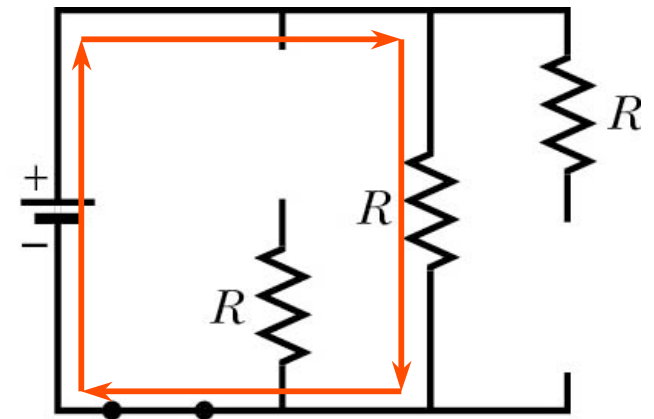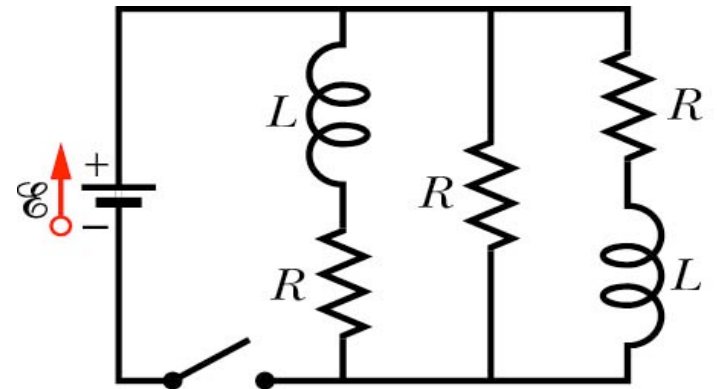

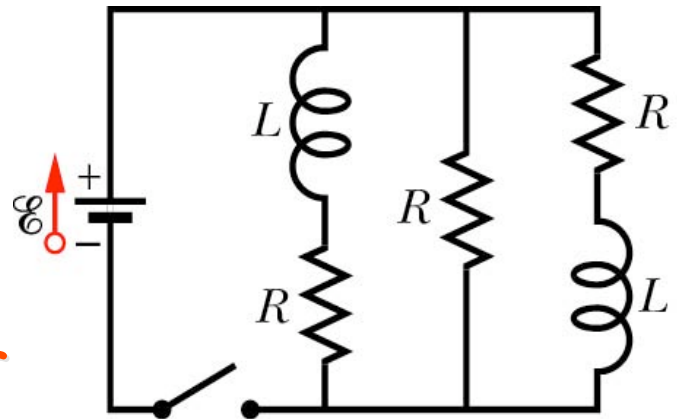Problem 31-5, continued


- > What is the current through the battery a **long time after** the switch has been closed?
- > Currents in circuit have reached equilibrium so **inductor acts like simple wire**
- > Circuit is 3 resistors in parallel



$$i = \frac{\mathcal{E}}{R_{eq}}$$

$$R_{eq} = \frac{R}{3}$$

Remember the “water slides”

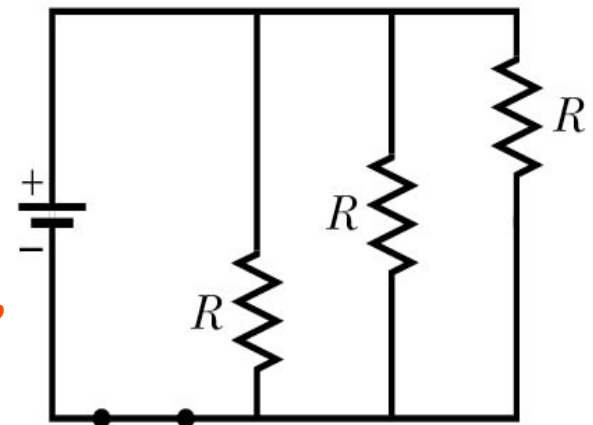

(c)


Energy

- > How much energy is stored in a B field?
- > Conservation of energy expressed in loop rule

$$\mathcal{E} = L \frac{di}{dt} + iR$$

- > Multiply each side by i
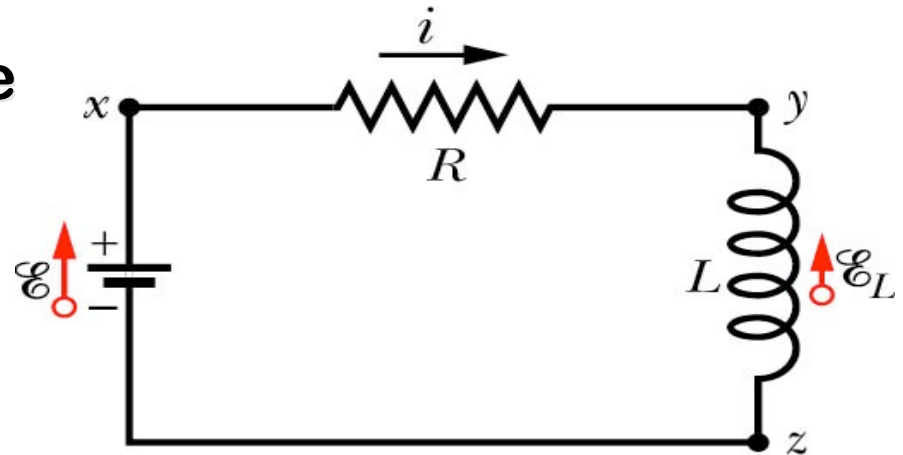
$$\mathcal{E}i = Li \frac{di}{dt} + i^2 R$$



- > $P=i\mathcal{E}$ is the rate at which the battery delivers energy to rest of circuit
- > $P=i^2 R$ is the rate at which energy appears as thermal energy in resistor

Energy (2)

- > Middle term is rate at which energy dU_B/dt is stored in the B field

$$\frac{dU_B}{dt} = Li \frac{di}{dt}$$

- > Energy stored in magnetic field

$$U_B = \frac{1}{2} Li^2$$

- > Similar to energy stored in electric field

$$U_E = \frac{1}{2} \frac{q^2}{C}$$

Energy Density

- > What is the energy density of a B field?
- > Energy density, u_B is energy per unit volume

$$u_B = \frac{U_B}{Al}$$

- > Magnetic energy density

$$u_B = \frac{1}{2} \frac{B^2}{\mu_0}$$

- > Similar to electric energy density

$$u_E = \frac{1}{2} \epsilon_0 E^2$$

Where does this come from?

$$B = \mu_0 n i$$

$$L = l \mu_0 n^2 A \Rightarrow$$

$$U_B = \frac{1}{2} i^2 L = \frac{1}{2} l \mu_0 n^2 i^2 A = \frac{1}{2} A l (n^2 i^2 \mu_0^2) / \mu_0$$

$$U_B / A l = \frac{1}{2} B^2 / \mu_0$$